


# Session 2 assignment



Q1) Design using Verilog HDL a 4-bit comparator circuit, with the following specifications:

- **Use** Always block.

Ports	Type	Size	Description
A	input	4-bit	--
B	input	4-bit	--
EN	input	1 bit	The comparator works when EN is high.
equal	output	1 bit	When A = B.
greater	output	1 bit	When A > B.
Less	output	1 bit	When A < B.

 

Q2) Design the following ALU (Arithmetic Logic Unit) using Verilog HDL, with the following specifications:

Ports	Type - Size	Description
A	Input – 4-bit	The first input port.
B	Input – 4-bit	The second input port.
cin	Input – 1 bit	Carry in, used only for addition operation.
opcode	Input – 2-bit	Operation code.
pass_A	Input – 1 bit	When it's high, pass A to out port and ignore the opcode.
pass_B	Input – 1 bit	When it's high, pass B to out port and ignore the opcode.
out	Output – 4-bit	The main output.
cout	Output – 1 bit	The carry out, it's equal zero for all operation instead of arithmetic operations

Note: **pass\_A** is the highest priority, the second is **pass\_B**, and the least is **opcode** operation

opcode signal	Operation
00	AND (A & B)
01	Addition (A + B)
10	Subtraction (A - B)
11	Reduction XOR operation on B

### Q3) Designing a Multi-bit Adder Using Module Instantiation

#### Tasks:

##### 1. Design a 1-bit Full Adder:

- Create a Verilog module named `full_adder`.
- Use one assign statement to compute the **Sum** and **Carry Out (Cout)**.  
Hint: use concatenation (curly braces).
- Inputs: **A, B, and Cin (carry-in)**.
- Outputs: Sum and Cout.

##### 2. Extend to a 2-bit Adder:

- Create a Verilog module named `adder_2bit`.
- Instantiate **two** `full_adder` modules inside `adder_2bit`.
- Connect them properly so that the carry propagates from **LSB to MSB**.  
Hint: (The first full adder generates an intermediate carry (**Cout\_1**), which is passed as the carry-in (**Cin**) to the second full adder. And the carry out of the `adder_2bit` will be the carry bit generated by the second full adder. This ensures correct addition of multi-bit numbers, allowing the carry to ripple through successive stages)
- Inputs: `A[1:0]`, `B[1:0]`, and `Cin`.
- Outputs: `Sum[1:0]` and `Cout`.

#### Submission Guidelines:

- The submitted file must be a **PDF file**.
- Name the file in the following format:  
**StudentName\_assignment2.pdf**
- The PDF must include:
  - Verilog design codes
  - Waveform snippets from **QuestaSim** showing test results.