

Assignment 3 – Model Answer

Q1)

ALU_tb code:

```

module ALU_tb;
    reg [3:0] A, B;
    reg pass_A, pass_B, cin;
    reg [1:0] opcode;
    wire [3:0] out;
    wire cout;

    ALU dut (A, B, pass_A, pass_B, cin, opcode, out, cout);

    task Validate_output ();
        if (pass_A) begin
            if (out != A) $display("Error: Pass A operation failed, pass_A: %d, A: %d, out: %d, Time: %0t", pass_A, A, out, $time);
        end
        else if (pass_B) begin
            if (out != B) $display("Error: Pass B operation failed, pass_B: %d, B: %d, out: %d, Time: %0t", pass_B, B, out, $time);
        end
        else begin
            case (opcode)
                2'b00: if(out != A&B) $display("Error: And operation failed, A: %d, B: %d, opcode: %d, out: %d, Time: %0t", A, B, opcode, out, $time);
                2'b01: if({cout, out} != A+B+cin) $display("Error: Addition operation failed, A: %d, B: %d, cin: %d, opcode: %d, out: %d, Time: %0t", A, B, cin, opcode, out, $time);
                2'b10: if({cout, out} != A-B) $display("Error: Subtraction operation failed, A: %d, B: %d, opcode: %d, out: %d, Time: %0t", A, B, opcode, out, $time);
                2'b11: if( out != ^B) $display("Error: Reduction XOR B operation failed, B: %d, opcode: %d, out: %d, Time: %0t", B, opcode, out, $time);
            endcase
        end
    endtask


    initial
        $monitor("A: %d, B: %d, pass_A: %d, pass_B: %d, cin: %d, opcode: %d, out: %d, cout: %d, Time: %0t", A, B, pass_A, pass_B, cin, opcode, out, cout, $time);

    initial begin
        A=0;
        B=0;
        pass_A=0;
        pass_B=0;
        cin=0;
        opcode=0;
        #10;

        repeat (100) begin
            A=$random;
            B=$random;
            pass_A=$random;
            pass_B=$random;
            cin=$random;
            opcode=$random;
            #10;
            Validate_output();
        end
        $stop;
    end
endmodule

```

Do file code:



```
vlib work
vlog ALU.v Model_Answer.v
vsim -voptargs=+acc work.ALU_tb
add wave *
run -all
#quit -sim
```

.....

Q2)

D_latch code:

```
module D_latch (
    input D, enable,
    output reg Q
);
    always @(*) begin
        if (!enable)
            Q = 0;
        else
            Q = D;
        end
    endmodule
```

D_latch_tb code:

```
module D_latch_tb;

    reg D, enable;
    wire Q;

    D_latch dut (D, enable, Q);


    task Validate_output();
        if (!enable) begin
            if (Q != 0) $display("Error: enable is desserted, enable: %d, D: %d, Q: %d,
Time: %0t", enable, D, Q, $time);
        end
        else begin
            if (Q != D) $display("Error: enable is asserted, enable: %d, D: %d, Q: %d,
Time: %0t", enable, D, Q, $time);
        end
    endtask

    initial
        $monitor("enable: %d, D: %d, Q: %d, Time: %0t", enable, D, Q, $time);

    initial begin
        enable = 0;
        D = 0;
        #10;

        repeat (100) begin
            enable=$random;
            D=$random;
            #10;
            Validate_output();
        end
        $stop;
    end
endmodule
```

Do file code:



```
vlib work
vlog D_latch.v D_latch_tb.v
vsim -voptargs=+acc work.D_latch_tb
add wave *
run -all
#quit -sim
```


Q3)

D_t_ff:


```
module d_t_flipflop (  
    D, rst_n, clk, Q, Qbar  
);  
    parameter FF_TYPE = "DFF";  
    input D, rst_n, clk;  
    output reg Q;  
    output Qbar;  
    assign Qbar = ~Q;  
    always @(posedge clk or negedge rst_n) begin  
        if (~rst_n)  
            Q <= 1'b0;  
        else begin  
            if ("DFF" == FF_TYPE)  
                Q <= D;  
            else if (D)  
                Q <= ~Q;  
        end  
    end  
end  
endmodule
```

Q4)


reg_blocking:

 

reg_nonblocking:

 

comb_blocking:

 

comb_nonblocking::

